




**Dhirubhai Ambani Institute of Information
and Communication Technology**

EL114

Digital Logic Design

Dr. Yash Agrawal
Assistant Professor,
DA-IICT, Gandhinagar

Level of Abstraction

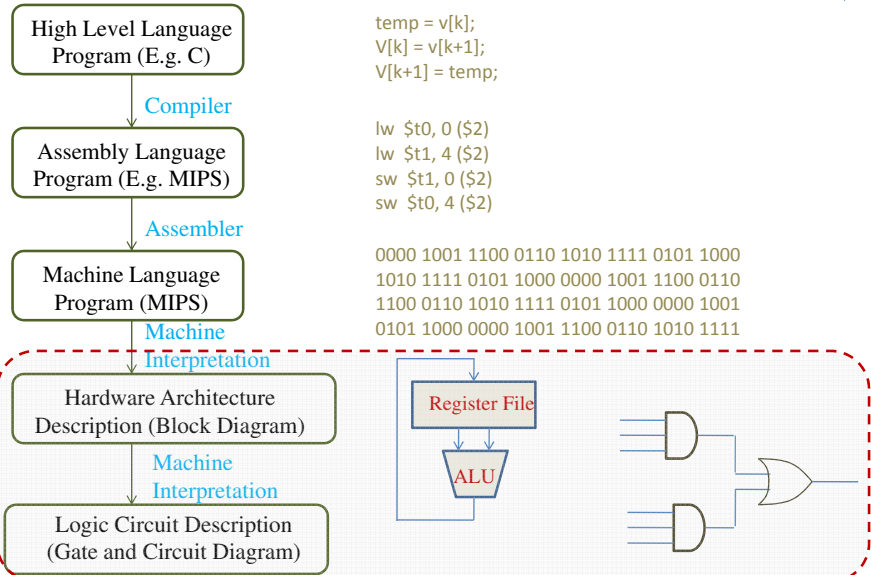

Dr. Yash Agrawal @ DA-IICT Gandhinagar

2

Introduction

What is
Combinational
&
Sequential
Concept...?

Dr. Yash Agrawal @ DA-IICT Gandhinagar

3

Logical Interpretation

Combinational vs. Sequential

1. Concept of Execution



Dr. Yash Agrawal @ DA-IICT Gandhinagar

4


Combinational vs. Sequential

2. Concept of Memory



Combinational vs. Sequential

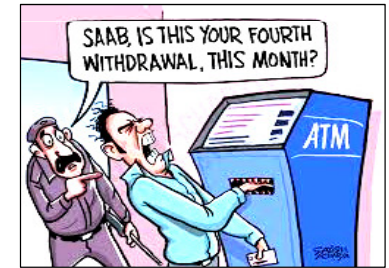
3. Concept of Input(s) Present/Requirement



Combinational vs. Sequential

1. Implement

$$S = A + B$$

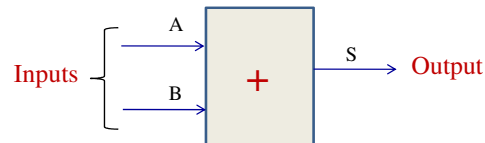

Combinational vs. Sequential

2. Implement

$$S = S + (A + B)_i$$

where i is integer and varying with time.

$$S = 0 \text{ at starting of time i.e. at } i = 0$$



$$S = 0$$

for $(i = 1, i < t, i = i + 1)$

$$S_i = S_{i-1} + (A + B)_i$$

Combinational vs. Sequential

2. Implement

$S = 0$
 for ($i = 1, i < t, i = i + 1$)
 $S_i = S_{i-1} + (A + B)_i$


Can You realize it using combinational logic...?

Combinational vs. Sequential

2. Implement using Sequential Logic

$S = 0$
 for ($i = 1, i < t, i = i + 1$)
 $S_i = S_{i-1} + (A + B)_i$


Does this work

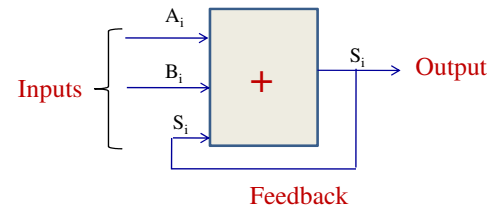

Combinational vs. Sequential

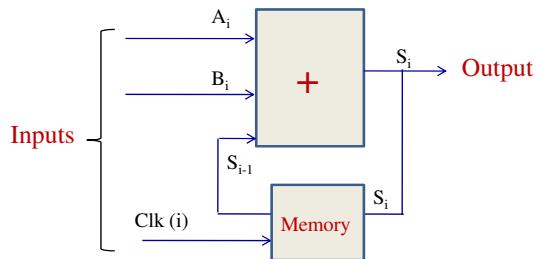2. Implement using Sequential Logic

$S = 0$
 for ($i = 1, i < t, i = i + 1$)
 $S_i = S_{i-1} + (A + B)_i$



Now validate the discussed points for sequential logic as in 'Logical Interpretation'.

- ✓ Concept of Execution
- ✓ Concept of Memory
- ✓ Concept of Input(s) Present/Requirement


Difference Between Combinational & Sequential Circuits

- Memory Requirement
- Clock/Enable Requirement
- Inputs
- Speed
- Design Complexity

Synchronous Systems

All operations are controlled by one central common clock signal.

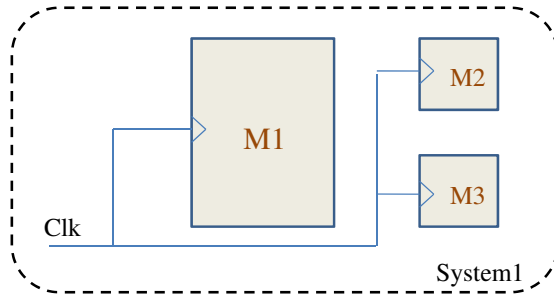
The clock signal is used to determine/control the exact time at which any output can change its state



Asynchronous Systems


Different modules are triggered by different clock/controlling signals.

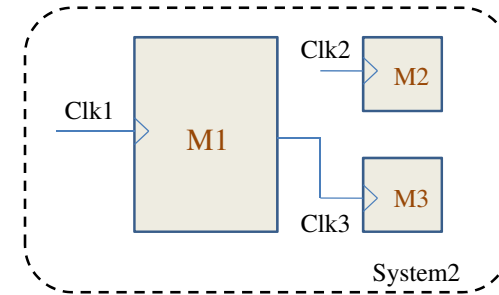In Asynchronous systems, the output of the logic circuit can change its state at any time, as soon as any input changes its state.




Numerical

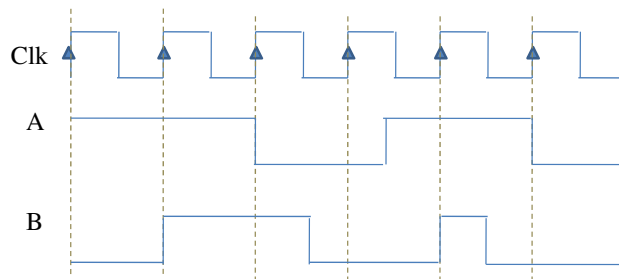- Determine the output of 2-input single-bit AND gate for the given set of inputs for the following cases
 - If the system is designed as Asynchronous.
 - If the system is designed as Synchronous.



Numerical

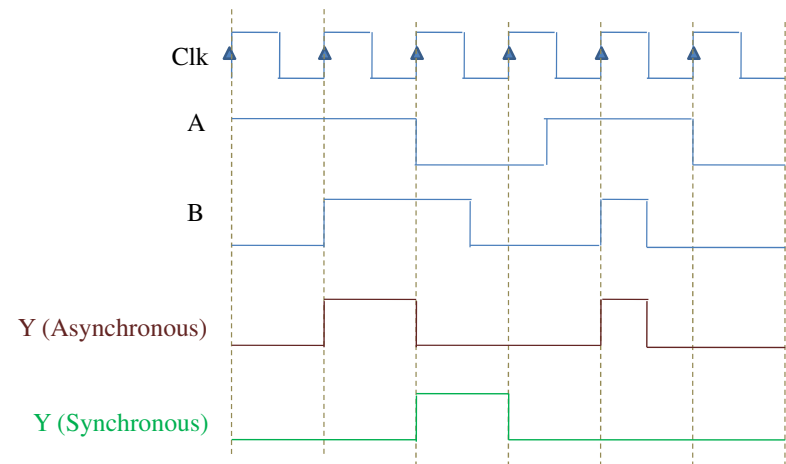

Control Signals

- Sequential circuits are dependent on the control trigger signals that are provided at its input.
- Depending on type of control signal, the output of the sequential circuit changes.
- There are four major control Trigger signals as

1. High Level Triggering


2. Low Level Triggering

3. Positive Edge Triggering


4. Negative Edge Triggering

Control Signals

1. High Level Triggering

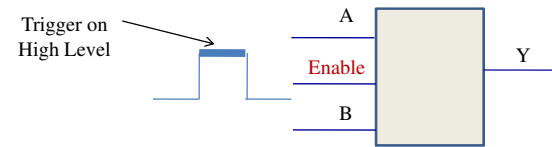


2. Low Level Triggering

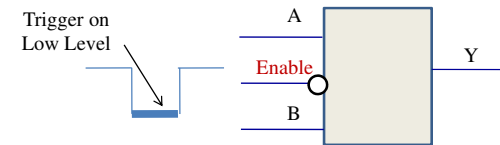


Control Signals


3. Positive Edge Triggering

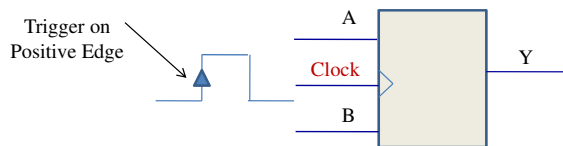

4. Negative Edge Triggering

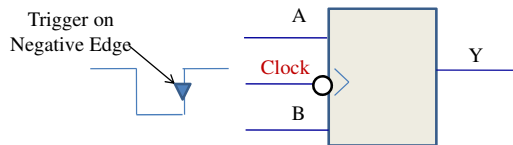

Sequential Circuit

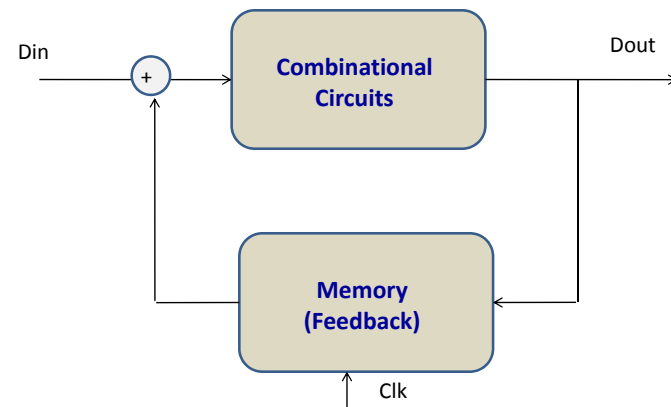

Types of latches and Flip-flops

- S-R
- D
- J-K
- T

Inter-conversion between different flip-flops

- Register
- Counter

Numericals

on

Sequential Circuits