




EL114

Digital Logic Design

Dr. Yash Agrawal
Assistant Professor,
DA-IICT, Gandhinagar

Introduction


Combinational logic Circuit

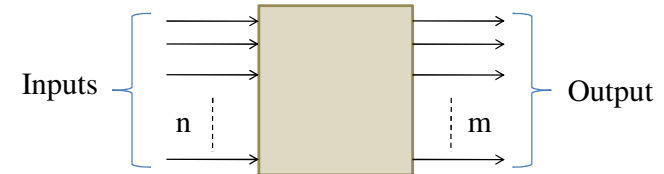

Encoder


Encoder:

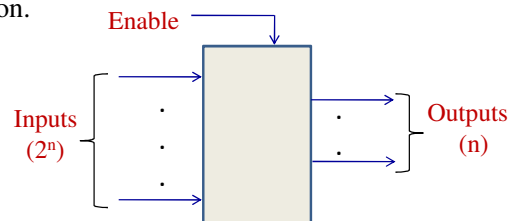- '2ⁿ' inputs to 'n' outputs.
- It has no select lines.
- Usually single input is assumed to be high. If more than one input is high, then Priority Encoder is used.
- Used in many applications such as memory system, code conversion, implementation of function.



Encoder Example

4:2 Encoder:

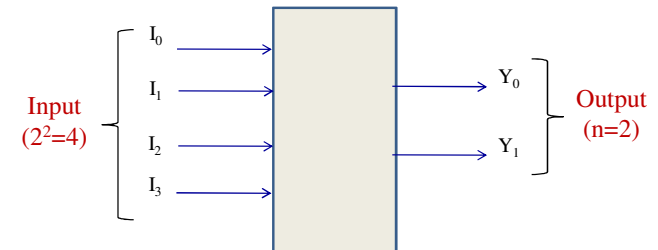

4:2 Encoder

First Step: Truth Table Formation

Input of Encoder				Output of Encoder	
I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

4:2 Encoder

Second Step: Determining Boolean Expression

Input of Encoder				Output of Encoder	
I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1




$$Y_0 = I_1 + I_3$$

$$Y_1 = I_2 + I_3$$


4:2 Encoder

Third Step: Realization of Boolean Expression by Logic Gates

$$Y_0 = I_1 + I_3$$

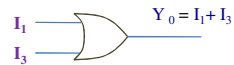

$$Y_1 = I_2 + I_3$$

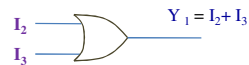

4:2 Encoder

What if more than one input is High...?

Input of Encoder				Output of Encoder	
I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	1		
0	1	0	0		
0	1	1	0		
1	1	1	1		



4:2 Priority Encoder

The ambiguity for cases when inputs are High for more than at one place can be solved by assigning priority (P).

First Step:
Truth Table Formation

Input of Encoder				Output of Encoder		
I_3	I_2	I_1	I_0	P	Y_1	Y_0
0	0	0	0	0	x	x
0	0	0	1	1	0	0
0	0	1	x	1	0	1
0	1	x	x	1	1	0
1	x	x	x	1	1	1

4:2 Priority Encoder

Second Step:
Determining Boolean Expression
(For this K-map can be used)

K-map and Boolean Expression determination for Y_0

$I_3 I_2$	$I_1 I_0$	00	01	11	10
00	x	m0	m1	1	1
01	m4	m5	m7	m6	
11	1	1	1	1	
10	1	1	1	1	

$$Y_0 = I_2' I_1 + I_3$$

Input of Encoder				Output of Encoder		
I_3	I_2	I_1	I_0	P	Y_1	Y_0
0	0	0	0	0	x	x
0	0	0	1	1	0	0
0	0	1	x	1	0	1
0	1	x	x	1	1	0
1	x	x	x	1	1	1

4:2 Priority Encoder

Second Step:
Determining Boolean Expression
(For this K-map can be used)

K-map and Boolean Expression determination for Y_1

$I_3 I_2$	$I_1 I_0$	00	01	11	10
00	x	m0	m1	m3	m2
01	1	1	1	1	
11	1	1	1	1	
10	1	1	1	1	

$$Y_1 = I_2 + I_3$$

Input of Encoder				Output of Encoder		
I_3	I_2	I_1	I_0	P	Y_1	Y_0
0	0	0	0	0	x	x
0	0	0	1	1	0	0
0	0	1	x	1	0	1
0	1	x	x	1	1	0
1	x	x	x	1	1	1

4:2 Priority Encoder

Second Step:
Determining Boolean Expression
(For this K-map can be used)

K-map and Boolean Expression determination for P

$I_3 I_2$	$I_1 I_0$	00	01	11	10
00	m0	1	1	1	
01	1	1	1	1	
11	1	1	1	1	
10	1	1	1	1	

$$P = I_0 + I_1 + I_2 + I_3$$

Input of Encoder				Output of Encoder		
I_3	I_2	I_1	I_0	P	Y_1	Y_0
0	0	0	0	0	x	x
0	0	0	1	1	0	0
0	0	1	x	1	0	1
0	1	x	x	1	1	0
1	x	x	x	1	1	1


4:2 Priority Encoder

Third Step:
Realization of Boolean Expression
by Logic Gates

$$Y_0 = I_2' I_1 + I_3$$


$$Y_1 = I_2 + I_3$$

$$P = I_0 + I_1 + I_2 + I_3$$

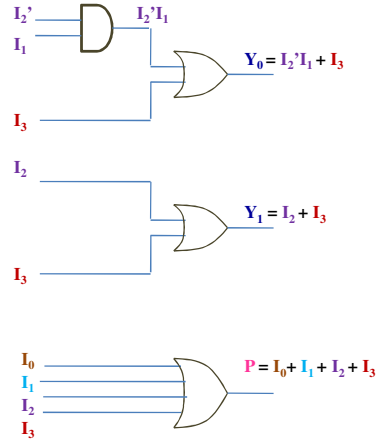

Encoder Example

8:3 Encoder:

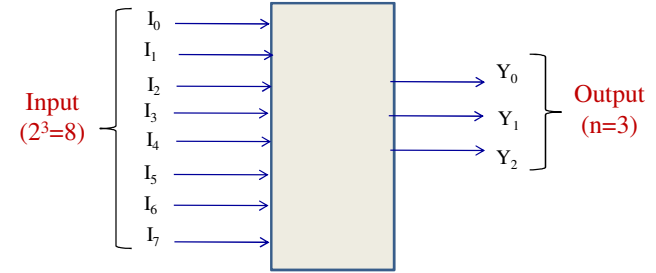

8:3 Encoder

First Step:
Truth Table Formation

Input of Encoder								Output of Encoder		
I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8:3 Encoder

Second Step:
Determining Boolean Expression

Input of Encoder								Output of Encoder		
I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1



$$Y_0 = I_1 + I_3 + I_5 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$




$$Y_2 = I_4 + I_5 + I_6 + I_7$$

Third Step: Realization of Boolean Expression by Logic Gates

$$Y_0 = I_1 + I_3 + I_5 + I_7$$

$$Y_1 = I_2 + I_3 + I_6 + I_7$$

$$Y_2 = I_4 + I_5 + I_6 + I_7$$

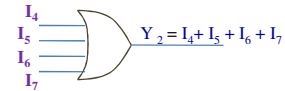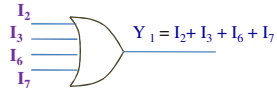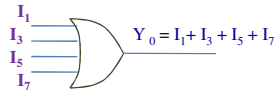


1. Implement Octal to Binary Encoder using 8:3 Encoder.
It should be able to convert from $(0)_8$ to $(7)_8$.

For example: $(4)_8 = (100)_2$

Implementation of Octal to Binary Encoder using 8:3 Encoder.

Octal Number	Input								Output		
Oct	I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	1	0	0	0	1
2	0	0	0	0	0	1	0	0	0	1	0
3	0	0	0	0	1	0	0	0	0	1	1
4	0	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	0	0	0	0	1	0	1
6	0	1	0	0	0	0	0	0	1	1	0
7	1	0	0	0	0	0	0	0	1	1	1

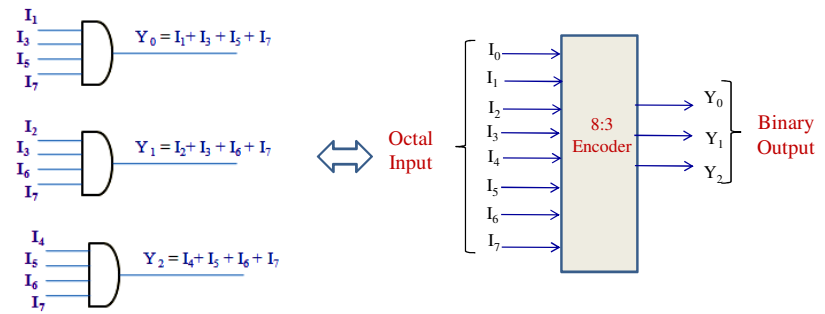Implementation of Octal to Binary Encoder using 8:3 Encoder.



Assignment-5

1. Realize 8:3 Priority Encoder.