



Dhirubhai Ambani Institute of Information
and Communication Technology


EL114

Digital Logic Design

Dr. Yash Agrawal
Assistant Professor,
DA-IICT, Gandhinagar

Introduction

Combinational logic Circuit

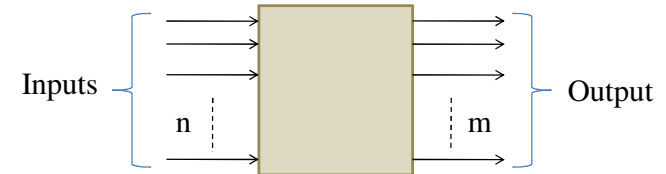

Dr. Yash Agrawal @ DA-IICT Gandhinagar

2

Demultiplexer (DeMUX)


Demultiplexer:

One input to Many outputs.

The Output line is selected based on the select line(s).

The outputs are in the form of 2^n , where n is the select line.

Used in many switching applications.

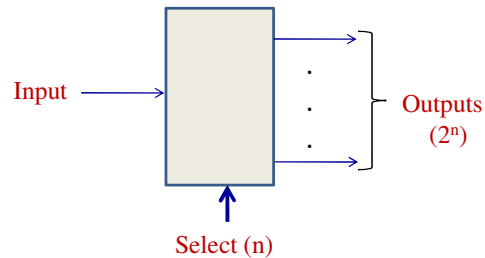


Dr. Yash Agrawal @ DA-IICT Gandhinagar

3

Demultiplexer Example

1:2 Demultiplexer:

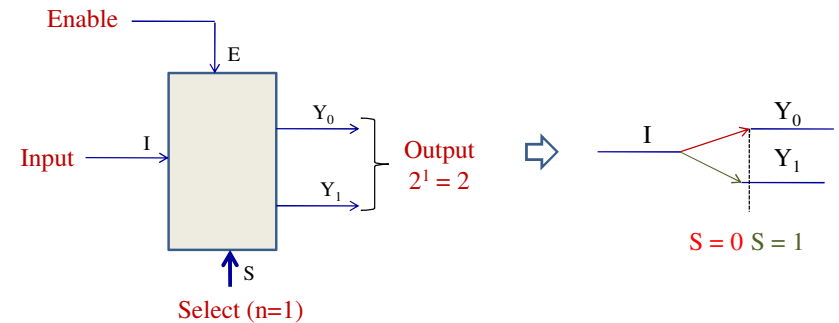


Dr. Yash Agrawal @ DA-IICT Gandhinagar

4


Demultiplexer Example

1:2 Demultiplexer:

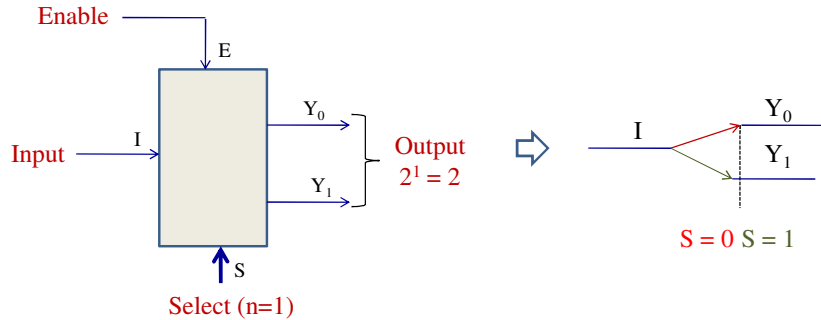

Demultiplexer Example

1:2 Demultiplexer:

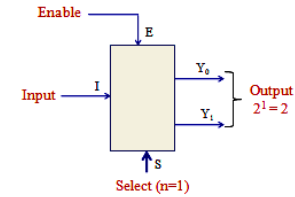

Number of Inputs = 3 (E, S, I)




Number of Input Combinations = $2^3 = 8$

Please Note: Enable is optional. And Many DeMUX may not have Enable input.

First Step: Truth Table Formation

Determined number
of inputs to be 3

Determined number
of outputs to be 2

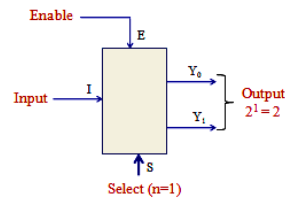

Inputs of 1:2 DeMUX Output of DeMUX

E	S	I	Y ₁	Y ₀
0	0	0	z/0	z/0
0	0	1	z/0	z/0
0	1	0	z/0	z/0
0	1	1	z/0	z/0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0



E	S	output
0	0	z/0
0	1	z/0
1	0	Y ₀
1	1	Y ₁

1:2 Demultiplexer

Second Step: Determining Boolean Expression (For this K-map can be used)

K-map and Boolean Expression
determination for Y₀

E	SI			
	00	01	11	10
0	m0	m1	m3	m2
1	m4	1 m5	m7	m6

$$Y_0 = ES'I$$

E	S	I	Y ₁	Y ₀
0	0	0	z/0	z/0
0	0	1	z/0	z/0
0	1	0	z/0	z/0
0	1	1	z/0	z/0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

1:2 Demultiplexer

Second Step:
Determining Boolean Expression
(For this K-map can be used)

K-map and Boolean Expression
determination for Y_1

SI	00	01	11	10
E 0	m0	m1	m3	m2
1	m4	m5	1 m7	m6

$$Y_1 = ESI$$


E	S	I	Y_1	Y_0
0	0	0	z/0	z/0
0	0	1	z/0	z/0
0	1	0	z/0	z/0
0	1	1	z/0	z/0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

1:2 Demultiplexer

Third Step:
Realization of Boolean Expression by Logic Gates


$$Y_0 = ES'I$$

$$Y_1 = ESI$$

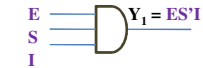


Demultiplexer Example

1:4 Demultiplexer:

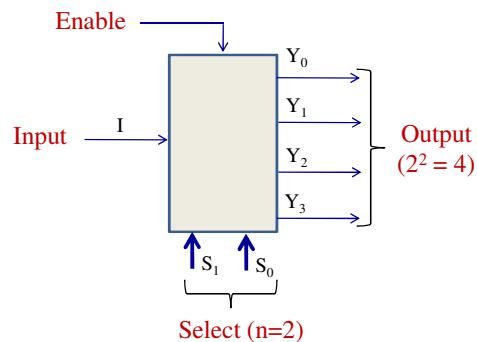

Demultiplexer Example

1:4 Demultiplexer:

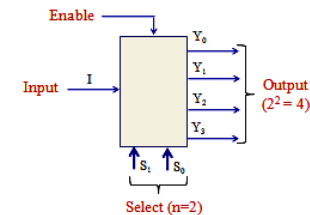

Number of Inputs = 4 (E, S_1 , S_0 , I)



Number of Input Combinations = $2^4 = 16$

Input of 1:4 DeMUX Output of DeMUX

First Step:
Truth Table Formation

Determined number
of inputs to be 4

Determined number of
outputs to be 4

E	S ₁	S ₀	I	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	0



E	S ₁	S ₀	output
0	x	x	0
1	0	0	Y ₀
1	0	1	Y ₁
1	1	0	Y ₂
1	1	1	Y ₃

1:4 Demultiplexer

Second Step:
Determining Boolean Expression

E	S ₁	S ₀	output
0	x	x	0
1	0	0	Y ₀
1	0	1	Y ₁
1	1	0	Y ₂
1	1	1	Y ₃



$$Y_0 = ES_1'S_0'I$$

$$Y_1 = ES_1'S_0I$$

$$Y_2 = ES_1S_0'I$$

$$Y_3 = ES_1S_0I$$

Dr. Yash Agrawal @ DA-IICT Gandhinagar

14

1:4 Demultiplexer



Third Step:
Realization of Boolean Expression
by Logic Gates

$$Y_0 = ES_1'S_0'I$$

$$Y_1 = ES_1'S_0I$$


$$Y_2 = ES_1S_0'I$$

$$Y_3 = ES_1S_0I$$

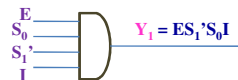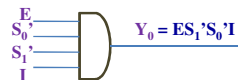

Demultiplexer Example

1:8 Demultiplexer:

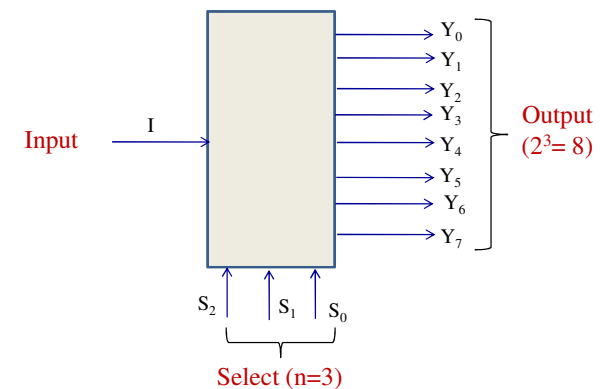

Dr. Yash Agrawal @ DA-IICT Gandhinagar

15

Dr. Yash Agrawal @ DA-IICT Gandhinagar

16

First Step: Truth Table Formation

S_2	S_1	S_0	Output
0	0	0	Y_0
0	0	1	Y_1
0	1	0	Y_2
0	1	1	Y_3
1	0	0	Y_4
1	0	1	Y_5
1	1	0	Y_6
1	1	1	Y_7

Second Step: Determining Boolean Expression


S_2	S_1	S_0	Output
0	0	0	Y_0
0	0	1	Y_1
0	1	0	Y_2
0	1	1	Y_3
1	0	0	Y_4
1	0	1	Y_5
1	1	0	Y_6
1	1	1	Y_7




$$\begin{aligned}
 Y_0 &= S_2' S_1' S_0' I \\
 Y_1 &= S_2' S_1' S_0 I \\
 Y_2 &= S_2' S_1 S_0' I \\
 Y_3 &= S_2' S_1 S_0 I \\
 Y_4 &= S_2 S_1' S_0' I \\
 Y_5 &= S_2 S_1' S_0 I \\
 Y_6 &= S_2 S_1 S_0' I \\
 Y_7 &= S_2 S_1 S_0 I
 \end{aligned}$$

Third Step: Realization of Boolean Expression by Logic Gates

$$\begin{aligned}
 Y_0 &= S_2' S_1' S_0' I \\
 Y_1 &= S_2' S_1' S_0 I \\
 Y_2 &= S_2' S_1 S_0' I \\
 Y_3 &= S_2' S_1 S_0 I \\
 Y_4 &= S_2 S_1' S_0' I \\
 Y_5 &= S_2 S_1' S_0 I \\
 Y_6 &= S_2 S_1 S_0' I \\
 Y_7 &= S_2 S_1 S_0 I
 \end{aligned}$$

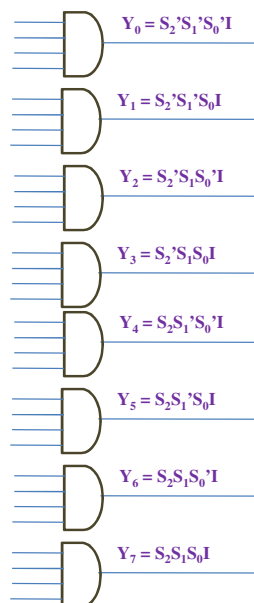

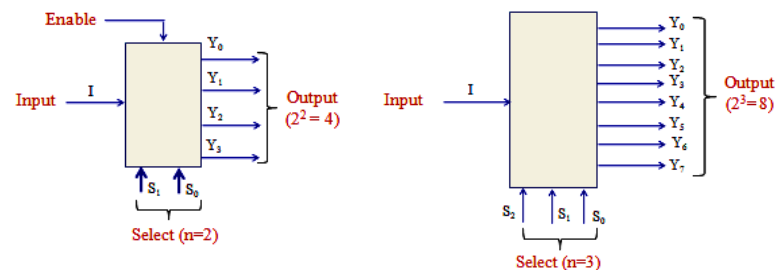Implement 1:8 Demultiplexer using 1:4 Demultiplexer




1:4 DeMUX
1 Input
2 Select lines
4 Output

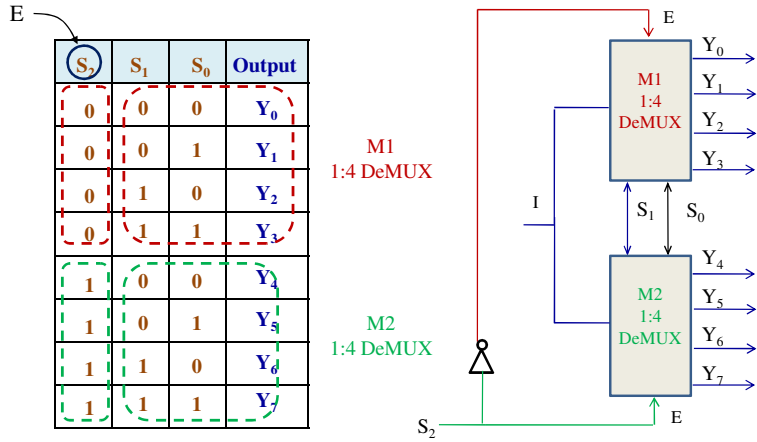1:8 DeMUX
1 Input
3 Select lines
8 Output

Implement 1:8 Demultiplexer using 1:4 Demultiplexer

To implementing 1:8 DeMUX using 1:4 DeMUX, Enable signal can be utilized



Numerical

1. Implement Full Subtractor using Demultiplexer.

First Step:
Truth Table Formation


A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Numerical

1. Implement Full Subtractor using Demultiplexer.

Second Step:
Realization using DeMUX

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

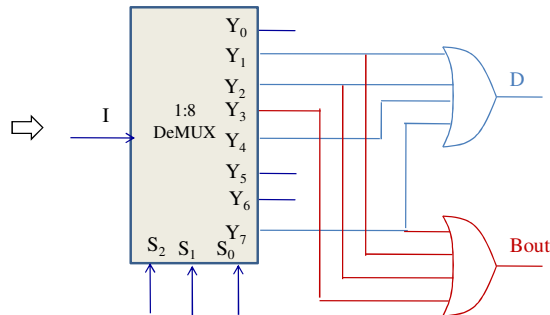

Assignment-4

1. Implement the following Boolean Function using 1:8 DeMUX (without using any Enable signal).

$$f(P, Q, R, S) = \sum m(0, 1, 3, 4, 8, 9, 15)$$