



Dhirubhai Ambani Institute of Information
and Communication Technology


EL114

Digital Logic Design

Dr. Yash Agrawal
Assistant Professor,
DA-IICT, Gandhinagar

Introduction

Sequential Circuit

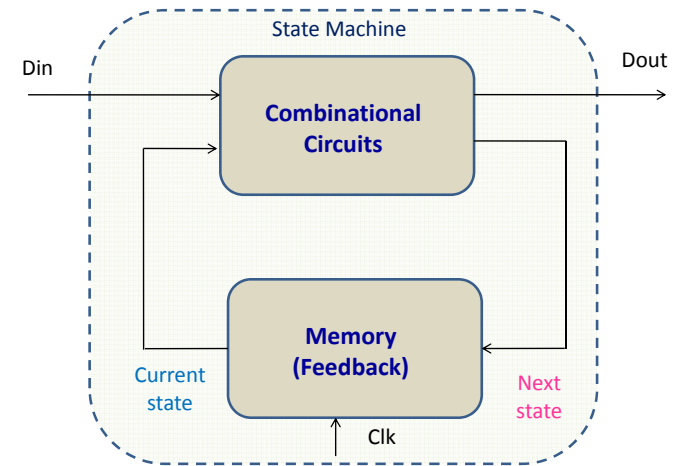

Dr. Yash Agrawal @ DA-IICT Gandhinagar

2

Introduction

How to realize Storage (Memory) Element

Dr. Yash Agrawal @ DA-IICT Gandhinagar

3

Basic Building Block for Storage/Memory

Latch

- Latch is level triggered single-bit memory element.
- Latch responds immediately to change in input(s) and (possibly in the presence of level enables control signal).
- Output can change multiple times during active enable (clock) signal.

Flip-flop

- Flip-flop is edge triggered single-bit memory element.
- Output can change only one time during clock cycle.

Dr. Yash Agrawal @ DA-IICT Gandhinagar

4

Latch vs. Flip-flop

What's the basic difference...?

Latch is **level-triggered**




Flip-flop is **edge-triggered**



Case I


Consider the Circuit

 

1. This circuit is level triggered or edge triggered?

Case I


Consider the Circuit

 

2. What do you mean by edge triggered?
3. How circuit can operate at edge of control signal?
4. Fundamentally, how circuit see level/edge triggering?

Case I

Consider the Circuit

 


5. How to operate the same circuit as in level triggered or edge triggered configuration?

Case II

Consider the Circuit

Let initially $Q = 0$

 

- As long as $\text{Clk} = 1$, the value of Q continues to change.
- The change are based on the delay present on the loop through the connection from Q to Q .
- This behavior is unacceptable not desirable.
- **Desired Behavior: Q changes only once clock pulse**

Case II

Consider the Circuit

Let initially $Q = 0$



What to do...?

The solution to the latch timing issue is to **break** the closed path from Q to Q within the storage element.

Basic Building Block for Storage/Memory

Issues in Case I and Case II


1. How edge triggering concept can be executed...?
2. How to break closed path?

Solutions to both Case I and Case II

1. Pulse Generator
2. Master-Slave Configuration


Basic Building Block for Storage/Memory

1. Pulse Generation

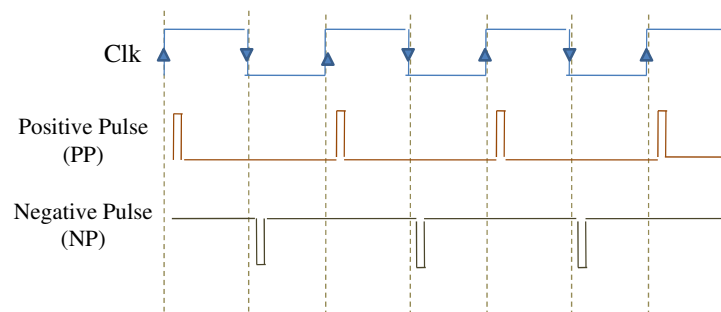


* The pulse width \leq propagation delay (t_p) of flip-flop

Positive Pulse Forming Circuit

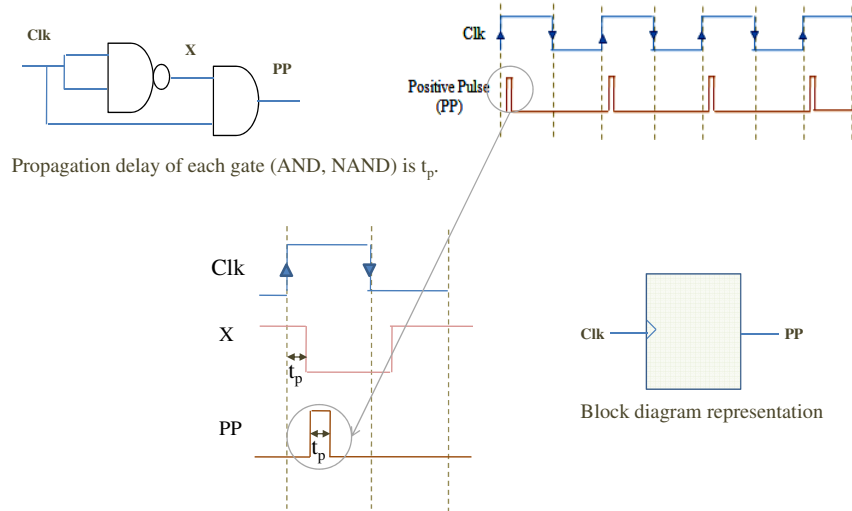


Negative Pulse Forming Circuit

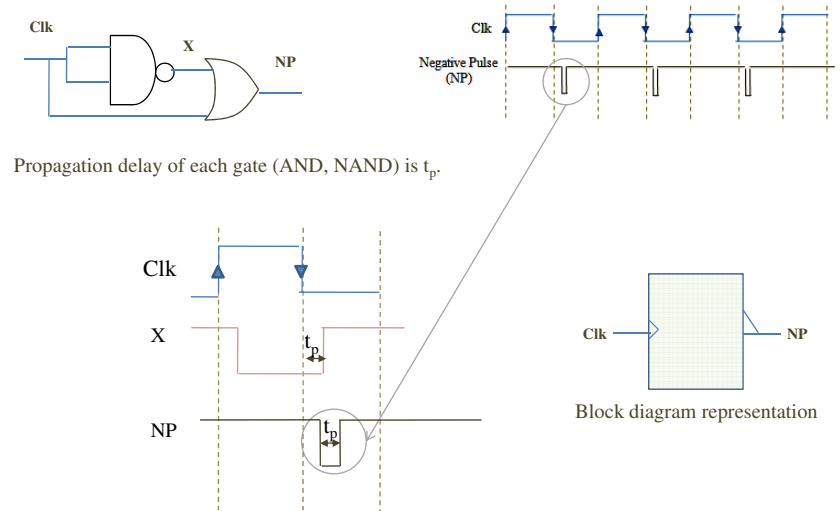

Basic Building Block for Storage/Memory


2. Master-Slave Configuration

Consider the Circuit

 

Basic Hardware Designs for Storage/Memory Element

Master-Slave Configuration

 

Types of Flip-flop

Different Flip-flops that will be discussed are:

- S-R
- D
- J-K
- T


S-R Flip-flop

S-R Flip-flop is known as SET-RESET Flip-flop.


It can be used to either Set/Reset output or store previous value.

Basic Hardware Designs for Storage/Memory Element


Cross-coupled NORs
(S-R Latch)

 


Cross-coupled NANDs
(S'-R' Latch)

 

Gated S-R Latch

 


How to implement S-R Flip-flop...?

 


Will it work...?

 Basic Hardware Designs for Storage/Memory Element




Clock control signal is used

S-R Flip-flop

 


Using pulse generator

 


Using Master-Slave configuration


S-R Flip-flop

 

Circuit diagram

 

Block diagram

 

Block diagram

Truth Table


Input of Flip-Flop			Output of flip-flop	
Clk	S	R	Q_{n+1}	State
↑	0	0	Previous State	No Change
↑	0	1	0	Reset
↑	1	0	1	Set
↑	1	1	Undefined	Forbidden
0	x	x	Previous State	No Change

* Q'_{n+1} is complementary to Q_{n+1} .

S-R Flip-flop

Characteristic Table


Inputs of FF			Output of FF
S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x

 

Circuit diagram


Characteristic equation

Determination of Q_{n+1} using K-map

 

$$Q_{n+1} = S + R'Q_n$$

S-R Flip-flop

 

Circuit diagram

Characteristic Table

Inputs of FF			Output of FF
S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x


Excitation Table

Output of FF		Input of FF	
Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

D Flip-flop


- D flip-flop is also known as Delay and Transparent flip-flop.
- It is derived from S-R flip-flop where 'R' input is inverted of 'S' input.
- In D flip-flop '00' or '11' doesn't exist. Hence, there is no indefinite/forbidden condition.
- D flip-flop is often used as a 1-bit memory element.

Gated D Latch

 


How to implement D Flip-flop...?


D Flip-flop

 

D Flip-flop

 

D Flip-flop

 


Truth Table

Input of FF		Output of FF	
Clk	D	Q_{n+1}	State
↑	0	0	Reset
↑	1	1	Set
0	x	Previous State	No Change

* Q'_{n+1} is complementary to Q_{n+1} .

D Flip-flop

 

Characteristic Table


Input of FF		Output of FF	
D	Q_n	Q_{n+1}	
0	0	0	
0	1	0	
1	0	1	
1	1	1	

Characteristic equation

Determination of Q_{n+1} using K-map

$$Q_{n+1} = D$$

D Flip-flop

 

Characteristic Table

Input of FF		Output of FF	
D	Q_n	Q_{n+1}	
0	0	0	
0	1	0	
1	0	0	
1	1	1	


Excitation Table

Output of FF		Input of FF
Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

J-K Flip-flop

- J-K flip-flop is proposed by **Jack-Kilby**.
- It is derived from S-R flip-flop where feedback is provided to overcome forbidden (11) condition. Here Q' is connected to J and Q to K.

S-R Flip-flop

 


Input of FF		Output of flip-flop	
Clk	S	R	Q_{n+1}
↑	0	0	Previous State
↑	0	1	0
↑	1	0	1
↑	1	1	Undefined
0	x	x	Previous State


This condition is undesirable
Leads to Race around condition

How to overcome it...?

J-K Flip-flop

 


Using pulse generator

 


Using Master-Slave configuration


J-K Flip-flop

 

Circuit diagram

 

Block diagram

 

Block diagram

Truth Table


Input of flip-flop			Output of Flip-flop	
Clk	J	K	Q_{n+1}	State
↑	0	0	Previous State	No Change
↑	0	1	0	Reset
↑	1	0	1	Set
↑	1	1	Complement of previous output Q'_n	Toggle
0	x	x	Previous State	No Change

* Q'_{n+1} is complementary to Q_{n+1} .

J-K Flip-flop

Characteristic Table

Inputs of FF		Output of FF	
J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 


Characteristic equation

Determination of Q_{n+1} using K-map

JK				
	00	01	11	10
0	m0	m2	1 m6	1 m4
1	1 m1	m3	m7	1 m5

$$Q_{n+1} = JQ'_n + K'Q_n$$

J-K Flip-flop

 

Characteristic Table

Inputs of FF		Output of FF	
J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


Excitation Table

Output of FF		Input of FF	
Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

T Flip-flop

- T flip-flop is also known as Toggle Flip-flop.
- It is derived from J-K flip-flop where J and K input terminals are shorted with each other.
- The T flip-flop doesn't exhibit 01' or '10' condition of J-K flip-flop.
- Owing to its continuous Toggling output generation, it is many times used for clock generation or as frequency divider circuit.


J-K Flip-flop

 


Input of flip-flop			Output of Flip-flop	
Clk	J	K	Q_{n+1}	State
↑	0	0	Previous State	No Change
↑	0	1	0	Reset
↑	1	0	1	Set
↑	1	1	Complement of previous output Q_n	Toggle
0	x	x	Previous State	No Change

Targeting these conditions


T Flip-flop

 


T Flip-flop

 

Circuit diagram

 

Block diagram

 


Block diagram

Truth Table

Input of FF		Output of Flip-flop	
Clk	T	Q_{n+1}	State
↑	0	Previous State	No Change
↑	1	Complement of Previous output Q_n	Toggle
0	x	Previous State	No Change

* Q'_{n+1} is complementary to Q_{n+1} .

T Flip-flop

 


Circuit diagram

Characteristic Table

Input of FF		Output of FF
T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0


Characteristic equation

Determination of Q_{n+1} using K-map

 

$$Q_{n+1} = Q_n T' + Q'_n T$$

T Flip-flop

 

Circuit diagram

Characteristic Table

Input of FF		Output of FF
T	Q_n	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table


Output of FF		Input of FF
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Asynchronous Flip-flops


- These have special inputs as preset (Pr) or clear (Cr).
- This are sometimes also referred as Direct inputs.

Asynchronous Flip-flops


S-R Flip-flop

 


D Flip-flop

 

J-K Flip-flop

 

T Flip-flop

 

Asynchronous Flip-flops



Truth Table

Direct Inputs		Output of Flip-flop	
Pr	Cr	Q_{n+1}	State
0	0	Undefined	Invalid
0	1	1	Preset
1	0	0	Clear
1	1	As per Flip-flop inputs	Normal operation

* Q'_{n+1} is complementary to Q_{n+1} .

Flip-flop Timing Constraints

Propagation delay

  


Flip-flop Timing Constraints

Setup Time (t_{setup}): Time before the clock edge for which data must remain stable (i.e. not changing).

Hold Time (t_{hold}): Time after the clock edge for which data must remain stable (i.e. not changing).

 Aperture Time (t_a): Time around the clock edge for which data must remain stable (it is sum of setup and hold time).




Applications of Flip-flop

- Memory design and data storage
- Logic control devices
- Shift registers
- Frequency division
- Counters

Exemplary Systems


1. Implementing N inputs adder

(using 2-input adder (s) only)

 

What can be other alternative...?


(using sequential serial approach)

 

Numerical

 1. Determine output if the given circuit as

- D- Latch (get triggered at active high level of clk signal)
- D-Flipflop (get triggered at rising edge of clk signal)



Numerical

Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

(Implement J-K Flip-flop using S-R flip-flop)

First Step: Write Required flip-flop at the LHS, then Q_n



Second Step: Determine Q_{n+1}



Third Step: From Excitation table, compute entire table



Fourth Step: Using K-map, determine inputs to the flip-flops.



Fifth Step: Realize the design.

Numerical

Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

First Step: Write Required flip-flop at the LHS, then Q_n

J	K	Q_n
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Numerical

Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

Second Step: Determine Q_{n+1}

J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Numerical

Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

Third Step: From Excitation table, compute entire table

J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	x
0	0	1	1	x	0
0	1	0	0	0	x
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	x	0
1	1	0	1	1	0
1	1	1	0	0	1

Excitation Table for SR FF

Output of FF		Input of FF	
Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

Numerical

Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

Fourth Step: Using K-map, determine inputs to the flip-flops.

J	K	Q_n	S	R
0	0	0	0	x
0	0	1	x	0
0	1	0	0	x
0	1	1	0	1
1	0	0	1	0
1	0	1	x	0
1	1	0	1	0
1	1	1	0	1

Boolean expression determination for 'S' using K-map

		JK			
		00	01	11	10
Q _n	0	m0	m2	1 m6	1 m4
	1	x m1	m3	m7	x m5

$$S = JQ'_n$$

Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

Fourth Step: Using K-map, determine inputs to the flip-flops.

J	K	Q_n	S	R
0	0	0	0	(x)
0	0	1	x	0
0	1	0	0	(x)
0	1	1	0	(1)
1	0	0	1	0
1	0	1	x	0
1	1	0	1	0
1	1	1	0	(1)

Boolean expression determination for 'R' using K-map

⇒

Q_n	JK			
	00	01	11	10
0	x m0	x m2		
1			1 m3	1 m7

$$R = KQ_n$$


Inter-conversion between different flip-flops

2. Convert S-R to J-K Flip-flop

Fifth Step: Realize the design.

$$S = JQ'_n$$

$$R = KQ_n$$

 

Assignment-8

1. Convert S-R to D Flip-flop.
2. Implement J-K Flip-flop using D Flip-flop.