



Dhirubhai Ambani Institute of Information  
and Communication Technology


EL114

## Digital Logic Design

Dr. Yash Agrawal  
Assistant Professor,  
DA-IICT, Gandhinagar

## Introduction

### Combinational logic Circuit

 


Dr. Yash Agrawal @ DA-IICT Gandhinagar

2

## Decoder
 
### Decoder:

- 'n' inputs to ' $2^n$ ' outputs.
- It has no select lines.
- Used in many applications such as memory system, code conversion, implementation of function.




Dr. Yash Agrawal @ DA-IICT Gandhinagar

3

## Decoder Example

### 2:4 Decoder:

 

Dr. Yash Agrawal @ DA-IICT Gandhinagar

4

## 2:4 Decoder

### First Step: Truth Table Formation

Input of Decoder		Output of Decoder			
$I_1$	$I_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

## 2:4 Decoder

### Second Step: Determining Boolean Expression

Input of Decoder		Output of Decoder			
$I_1$	$I_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0



$$Y_0 = I_1' \cdot I_0'$$

$$Y_1 = I_1' \cdot I_0$$

$$Y_2 = I_1 \cdot I_0'$$

$$Y_3 = I_1 \cdot I_0$$

## 2:4 Decoder


### Third Step: Realization of Boolean Expression by Logic Gates

$$Y_0 = I_1' \cdot I_0'$$

$$Y_1 = I_1' \cdot I_0$$


$$Y_2 = I_1 \cdot I_0'$$

$$Y_3 = I_1 \cdot I_0$$

 

## Decoder Example

### 3:8 Decoder:

 

### First Step: Truth Table Formation

Input of Decoder			Output of Decoder							
$I_2$	$I_1$	$I_0$	$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

### Second Step: Determining Boolean Expression

Input of Decoder			Output of Decoder							
$I_2$	$I_1$	$I_0$	$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0



$$Y_0 = I_2' \cdot I_1' \cdot I_0'$$

$$Y_1 = I_2' \cdot I_1' \cdot I_0$$

$$Y_2 = I_2' \cdot I_1 \cdot I_0'$$

$$Y_3 = I_2' \cdot I_1 \cdot I_0$$

$$Y_4 = I_2 \cdot I_1' \cdot I_0'$$

$$Y_5 = I_2 \cdot I_1' \cdot I_0$$

$$Y_6 = I_2 \cdot I_1 \cdot I_0'$$

$$Y_7 = I_2 \cdot I_1 \cdot I_0$$

## 3:8 Decoder

### Third Step: Realization of Boolean Expression by Logic Gates

$$Y_0 = I_2' \cdot I_1' \cdot I_0'$$

$$Y_1 = I_2' \cdot I_1' \cdot I_0$$

$$Y_2 = I_2' \cdot I_1 \cdot I_0'$$


$$Y_3 = I_2' \cdot I_1 \cdot I_0$$

$$Y_4 = I_2 \cdot I_1' \cdot I_0'$$

$$Y_5 = I_2 \cdot I_1' \cdot I_0$$

$$Y_6 = I_2 \cdot I_1 \cdot I_0'$$

$$Y_7 = I_2 \cdot I_1 \cdot I_0$$

 

## Numerical

- Implement the following Boolean function using
  - A Demultiplexer and external gates
  - A Decoder and external gates.

$$F1(A, B, C) = \sum m(1, 3, 5, 7)$$

$$F2(A, B, C) = \sum m(2, 3, 6, 7)$$


## Numerical

- Implement the following Boolean function using
  - A Demultiplexer and external gates
  - A Decoder and external gates.

$$F1(A, B, C) = \Sigma m(1, 3, 5, 7)$$

$$F2(A, B, C) = \Sigma m(2, 3, 6, 7)$$
 
### (i) Implementation using a Demultiplexer and external gates




## Numerical

- Implement the following Boolean function using
  - A Demultiplexer and external gates
  - A Decoder and external gates.

$$F1(A, B, C) = \Sigma m(1, 3, 5, 7)$$


$$F2(A, B, C) = \Sigma m(2, 3, 6, 7)$$
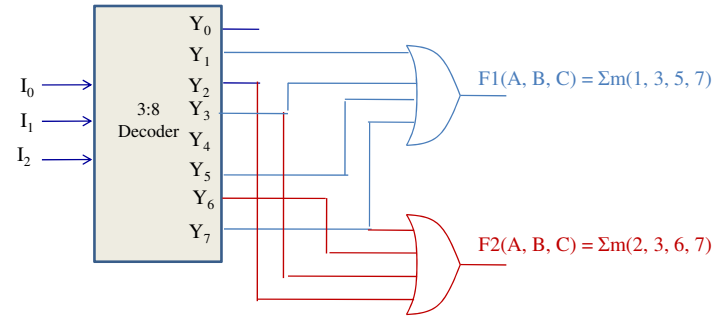
### (ii) Implementation using a Decoder and external gates



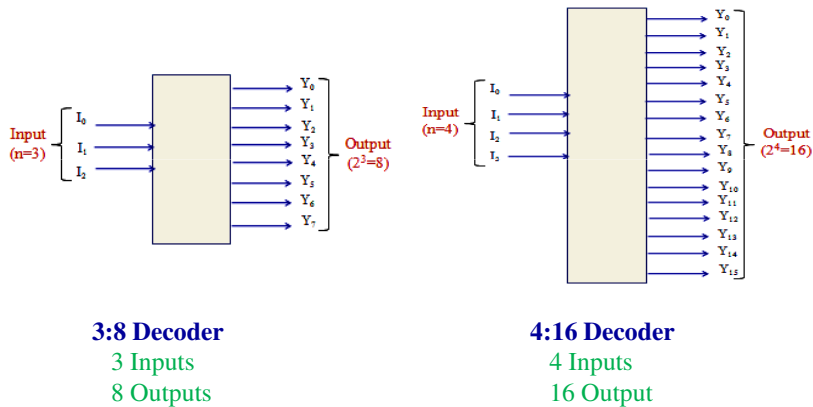
## Numerical

- Implement 4:16 Decoder using two 3:8 Decoders.


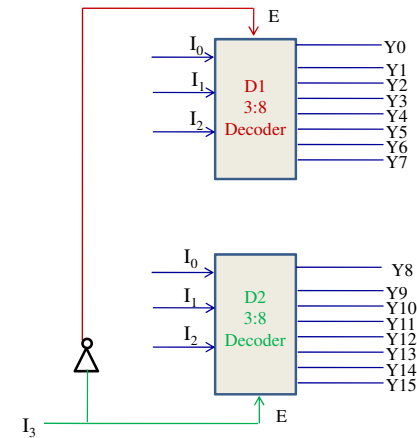
## Implement 4:16 Decoder using 3:8 Decoder

To implementing 4:16 Decoder using 3:8 Decoder, Enable signal can be utilized



## Assignment-6

1. Implement Full Adder using a suitable Decoder.
2. Implement 5:32 Decoder using 2:4 Decoder(s) and one 1:8 Demultiplexer.  
(More than one 2:4 decoders can be used)